

Bangladesh University of Engineering and Technology
Department of Computer Science and Engineering
CSE 206 - Digital Logic Design Sessional

Total Marks: 70

Duration: 60 minutes

Student Name:

Student ID:

(For Examiner’s Use Only)

1	2	3	4	5	6	7	8

Instructions

- 1. There are 5 Multiple Choice Questions and 5 True/False questions and 6 short questions in the script. Make sure all the questions are printed clearly before you start writing.
- 2. You should answer the all of the questions.

True/False Questions. Write T (for True) or F (for False) beside each of the question. [5]

- 1. a) The master latch of a positive edge-triggered master-slave D flip flop is active only during level 1 of the clock.

T

- b) Once an up/ down counter begins its count sequence, it cannot be reversed.

F

- c) You cannot use Priority Encoder as a normal encoder.

F

- d) You will need at least two 8x1 multiplexer and two 2x1 multiplexer to build a 16x1 multiplexer.

F

- e) The product-of-sums (POS) is basically the OR-ing of AND-ed terms.

F

2. a) You have the following chips: 7404, 7408, 7432, 74138. What are the minimum chips required to solve: $\sum (8,11,13,15)$?

- i. 1x74138, 1x7408

ii. 1x74138, 1x7432

✓ iii. 2x74138, 1x7408

iv. 2x74138, 1x7432

b) A MOD M and a MOD N up-counter when cascaded together results in a MOD _____ counter.


- i. M+N

ii. M-N

iii. M/N

✓ iv. M*N

 c) Assuming that the current state of the circuit (ABC) is 000, what will be the state of the circuit after 3 clock cycles?



- i. 111

✓ ii. 101

iii. 001

iv. 000

d) If the number of n selected input lines is equal to 2^m then it requires _____ select lines.

- i. 2

ii. n

✓ iii. m

iv. 2^n

e) How many gates would be required to implement the following Boolean expression after simplification?

$XY + X(X + Z) + Y(X + Z)$

- i. 1

✓ ii. 2

iii. 3

iv. 4

(idea from Zubayer Kayes Rafid) Boss

Short Questions

- Suppose you only have some 2 to 4 decoders and some 4 to 2 priority encoders with priority $0 < 1 < 2 < 3$. Now, you need a priority encoder with priority $3 < 2 < 1 < 0$. How would you implement this?

$\Rightarrow 0 < 1 < 2 < 3 \rightarrow$ Given

I_3	I_2	I_1	I_0	Y_1, Y_0	V
0	0	0	0	X X	0
0	0	0	1	0 0	1
0	0	1	X	0 1	1
0	1	X	X	1 0	1
1	X	X	X	1 1	1

Required ($3 < 2 < 1 < 0$)


I_0	I_1	I_2	I_3	Z_1, Z_0	V
0	0	0	0	X X	0
0	0	0	1	1 1	1
0	0	1	X	1 0	1
0	1	X	X	0 1	1
1	X	X	X	0 0	1

We see to get the required priority encoder

$$Z_1 = \bar{Y}_1 \quad Z_0 = \bar{Y}_0$$

$$\text{Now } Y_1 = I_3 + I_2$$


$$Y_0 = I_3 + I_1 \bar{I}_2$$

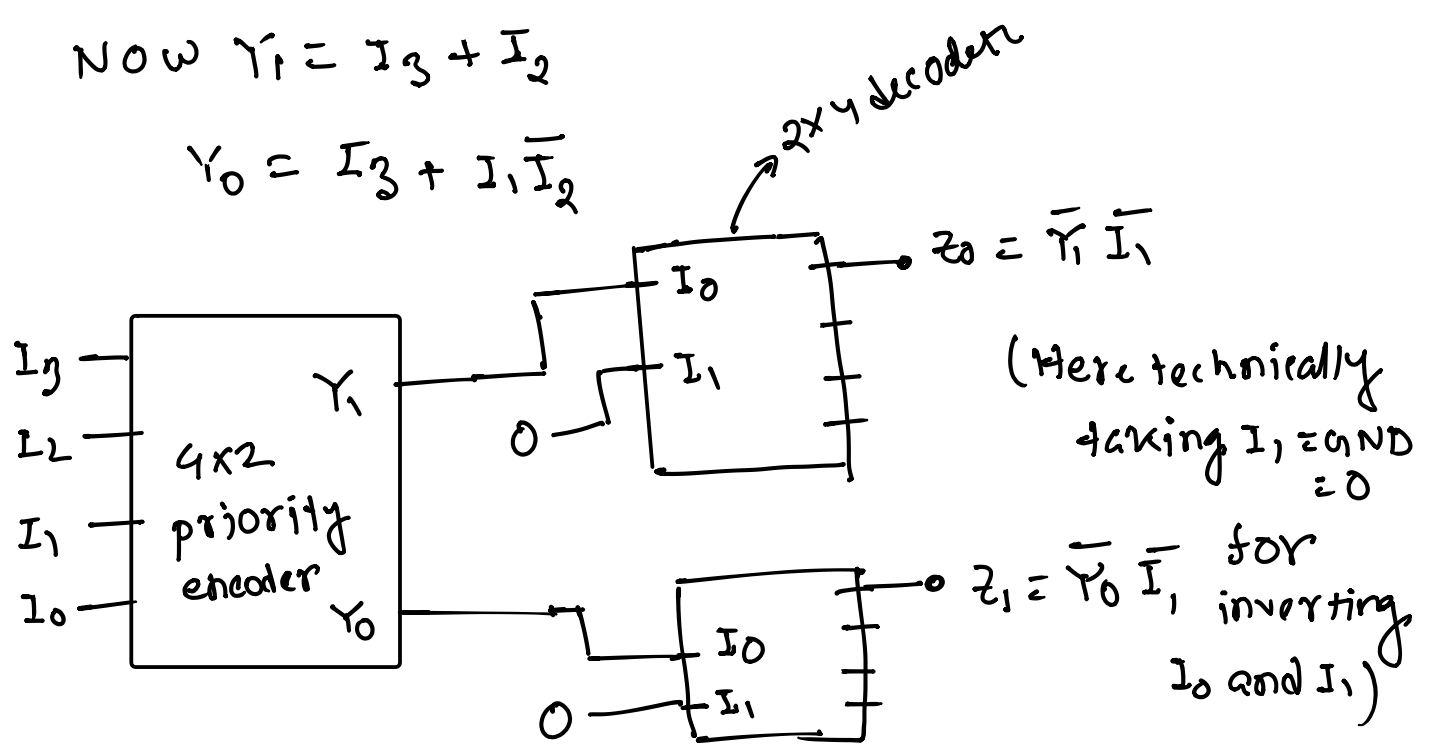

4. Suppose you have two 2-bit numbers A and B and an additional input bit C. When C is 0, you have to output the bitwise XOR of A and B. When C is 1, you have to output the bitwise XNOR of A and B. Design a combinational circuit using only half subtractors. You can assume to have access to VCC and GND. [10]



for a half subtractor

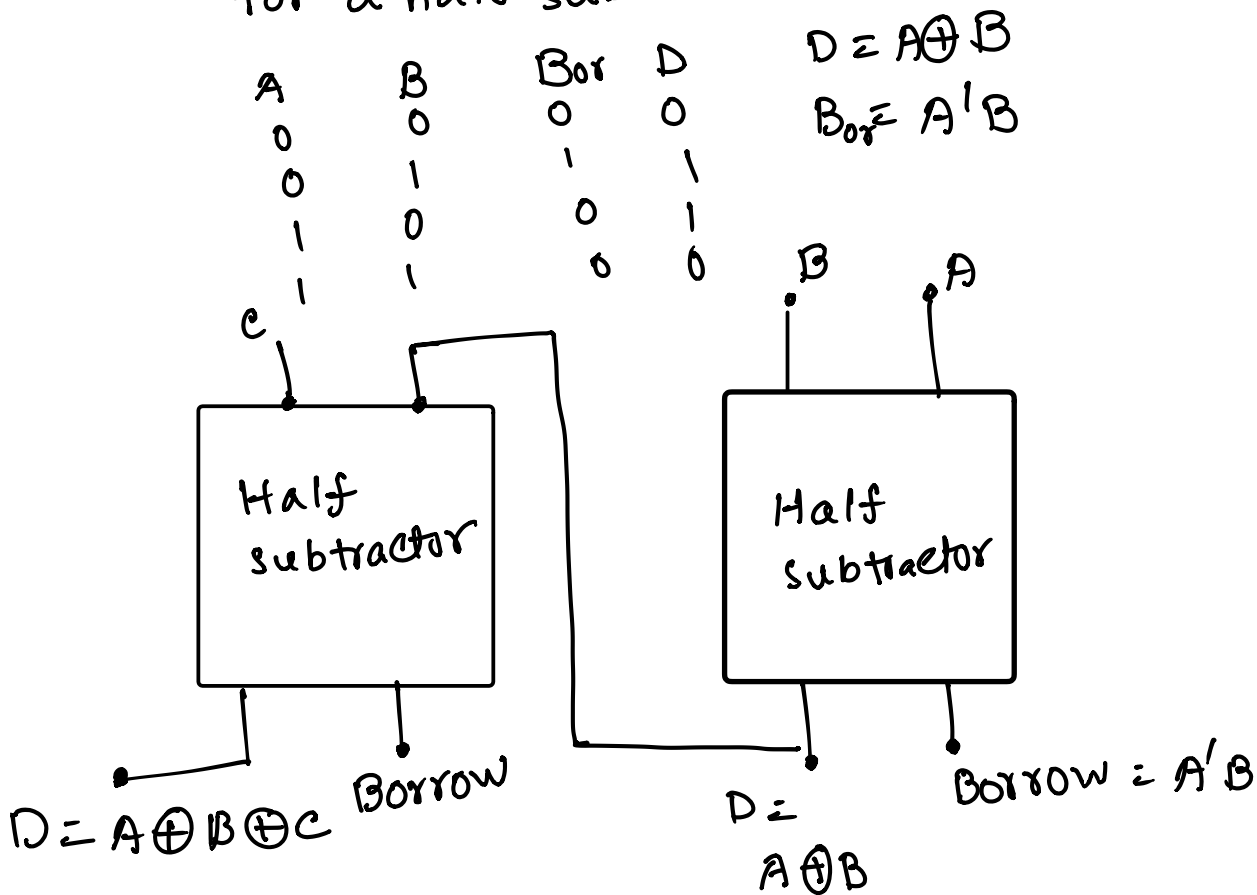

Now, if $c = 1$

$$D = (A \oplus B) \oplus 1 = \overline{A \oplus B}$$

$$\text{else } D = A \oplus B \oplus 0 = A \oplus B$$


5. Design an asynchronous MOD - 6 up/down counter using positive edge-triggered J-K flip-flops. The counter should have two modes of operation: down-counting when the mode bit M is set to 1, and up-counting when M is set to 0. [10]

$M = 0 \rightarrow$ up counter

$M = 1 \rightarrow$ down counter

reset when output is 6 = 110 (Hint XOR Q_2, Q_1)

 
for mod - 6 up/down counter, no of flip = $\lceil \log_2 6 \rceil = 3$



6. Simplify the function into the minimal SOP form using K-Map.

[10]

$$\Sigma(0,1,2,4,5,14,15) + d(6,7,8,9)$$

 

$$S = A'D' + A'C' + BC$$

- 7 A sequential circuit has two T flip-flops A and B, and an input x. The circuit can be described by the following input equations: [10]

$$T_A = Bx,$$

$$T_B = A'x$$

Derive the next state equations A_{t+1} and B_{t+1} . Also, draw the state diagram of this circuit.

$$\left. \begin{aligned} A_{t+1} &= T_A \oplus Q_A \\ B_{t+1} &= T_B \oplus Q_B \end{aligned} \right\} \begin{array}{l} \text{Because in the next state toggling} \\ \text{will occur if the input i.e., } T_A \text{ and} \\ T_B = 1 \end{array}$$

$$\begin{aligned} A_{t+1} &= Bx \oplus Q_A & \text{if } x=0; A_{t+1} &= Q_A; B_{t+1} &= Q_B \\ B_{t+1} &= A'x \oplus Q_B & \text{toggling will not occur} \end{aligned}$$


$$\text{else, } x=1; A_{t+1} = B \oplus Q_A = Q_B \oplus Q_A$$

$$B_{t+1} = A' \oplus Q_B = Q_A' \oplus Q_B$$

		NS			
		$x=0$		$x=1$	
	PS	A_{t+1}	B_{t+1}	A_{t+1}	B_{t+1}
$P =$	$Q_A \quad Q_B$	0	0	0	1
$Q =$	0	0	1	1	0
$R =$	1	1	0	1	0
$S =$	1	1	1	0	1

(Here $A = Q_A; B = Q_B$
present state
of the flipflop)

4 states

 

8. Designing NAND, NOR, XOR and XNOR Gates using minimum numbers of 2x1 multiplexers only. [10]

A	B	$(A \cdot B)'$	$(A + B)'$	$A \oplus B$	$\overline{A \oplus B}$
0	0	1	1	0	1
0	1	1	0	1	0
1	0	1	0	1	0
1	1	0	1	0	1

2x1 mux : A - selection bit

